

EE 234
EXPERIMENT # 6
BJT (Bipolar Junction Transistor) Characteristics

OBJECTIVE:

- To test the BJT transistor and identify its type and its three terminal leads.
- To study experimentally the static characteristics of forward and reverse biased 3904(plastic), 3906(plastic), & BC107 (metal) BJT transistors.
- To understand how to analysis practically the DC (V_C , V_B , V_E) and DC (I_C , I_B , I_E)
- To understand the Transistor modes of operations.

EQUIPMENT:

Breadboard /DMM /Avometer /FG /CRO/Curve Tracer / BJT transistors: 3904 (plastic), 3906 (plastic), & BC107 (metal).


PART (A): Testing BJT Type (NPN or PNP):

Procedure:


- To test the BJT type & identify its leads three terminals (Base, Emitter or Collector), we use the Avometer by the following procedure and filling the table below:
 - 1- We connect the (**positive**) lead of the Avometer with the mid lead terminals (Base₂) of the transistor and the other the (negative) lead of the Avometer to one end terminals (Emitter 1 or Collector 3) of the transistor.
 - 2- Measure resistance R and V, if we have large reading and zero voltage, we need to connect the (**negative**) lead of the Avometer with the mid lead terminals (Base₂).
 - 3- Measure resistance R and V, if we have small reading and ~ 0.8 V, then:
check the polarity of the Avometer that connect the (Base₂) terminal of the transistor (if its positive then its NPN transistor) & (if its negative then its PNP transistor).

Type	BC107 (metal)	3904(plastic)	3906(plastic)
NPN or PNP			




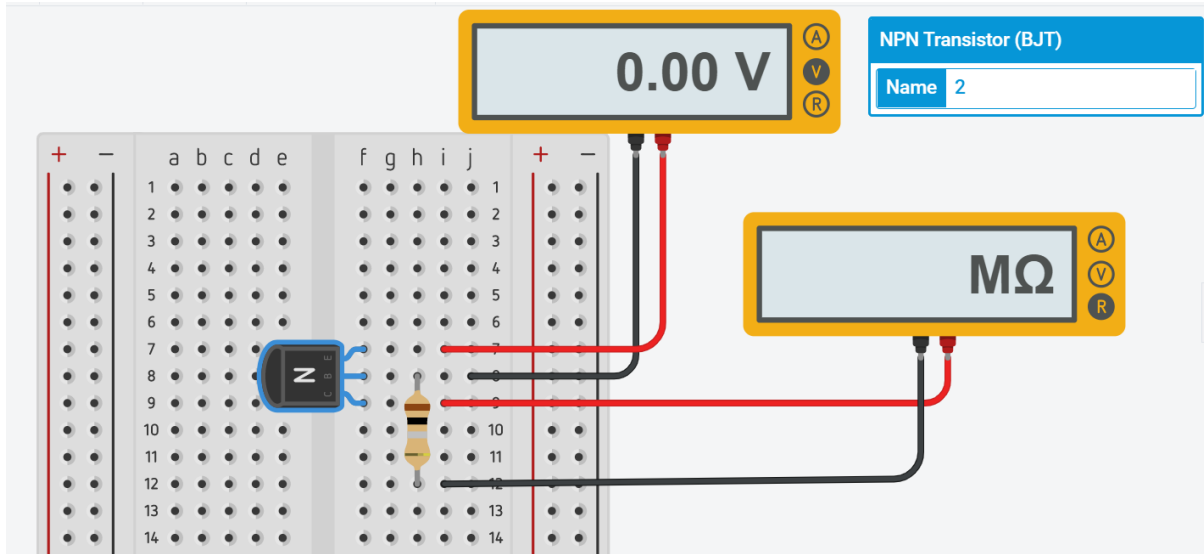


NPN for large reading

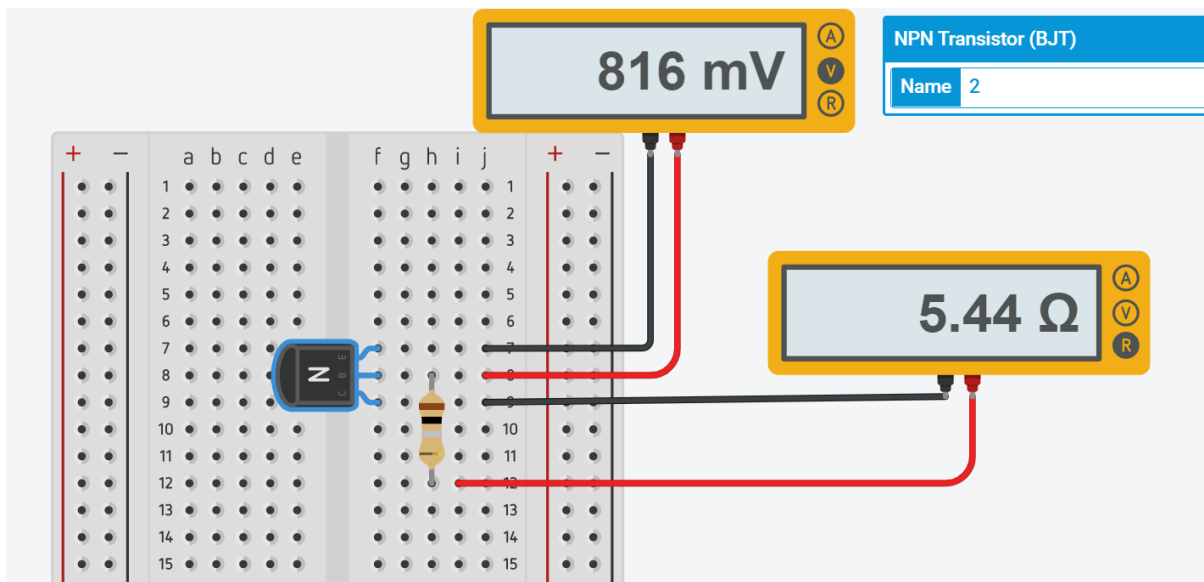

NPN for small reading

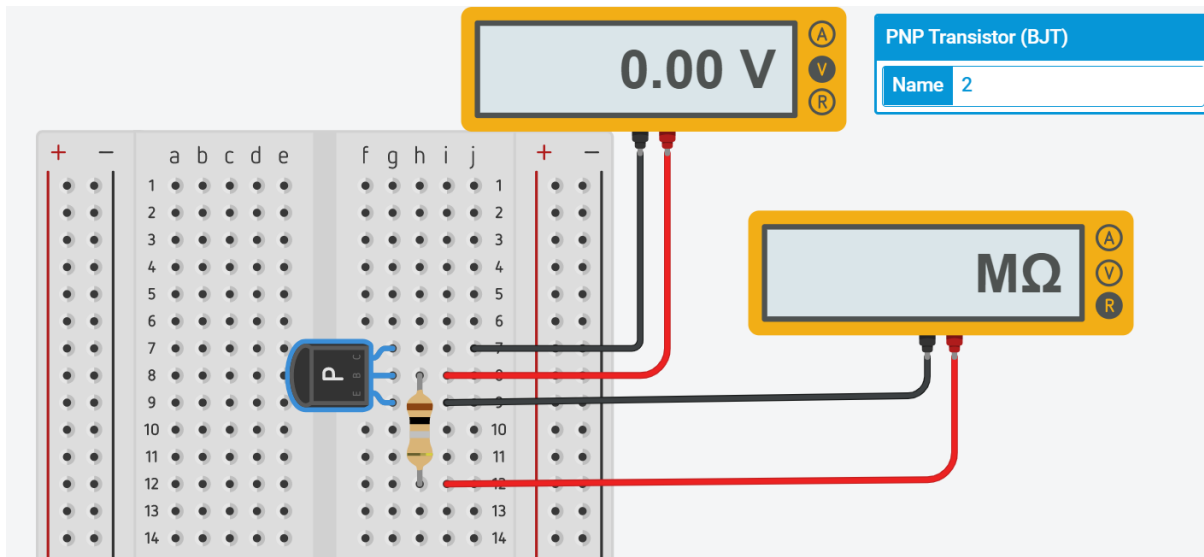

PNP for large reading

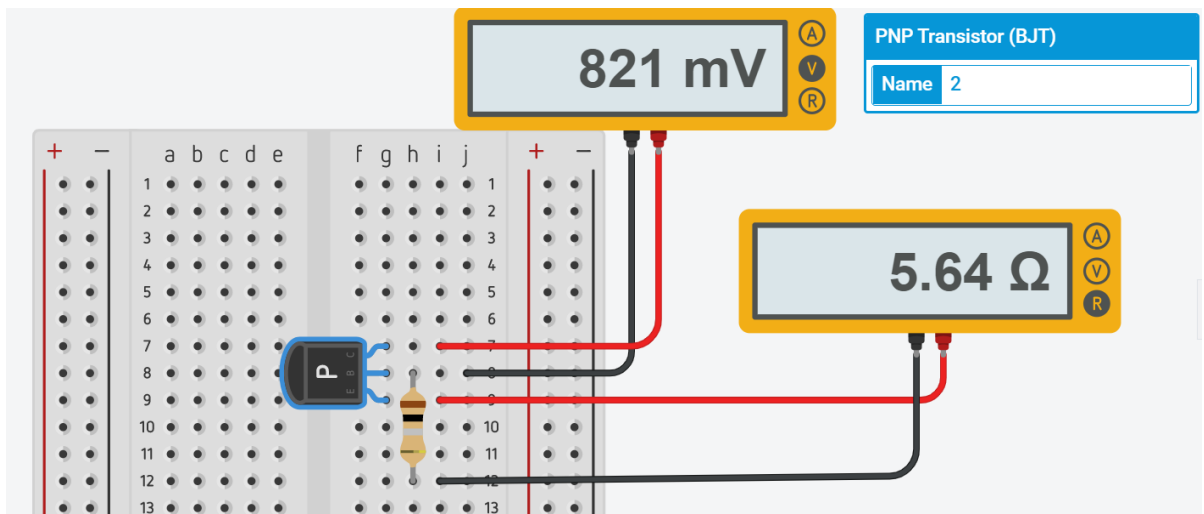

PNP for small reading

PART (B): The BJT Characteristics:

Procedure:

- Using the curve tracer in the lab room, we will obtain a curve between I_C & V_{CE} at different steps I_B of for the output characteristic of the BJT transistor & find h parameters values practically from the slope of the curve using the following formulas:
- $h_{fe} = \beta_{AC} = \Delta I_C / \Delta I_B \mid V_{CE} = \text{constant} = \dots > \alpha_{AC} = \beta_{AC} / (\beta_{AC} + 1) = \dots < 1$
- $h_{oe} = 1/r_o = \Delta I_C / \Delta V_{CE} \mid I_B = \text{constant} = \dots > r_o = \dots \Omega$
- Note: $h_{ie} = r_{\pi} = \Delta V_{BE} / \Delta I_B \mid V_{CE} = \text{constant} = \dots \Omega$. Will be obtained by the input characteristic of the BJT transistor using the curve submit by Engineer.

PART (C): Dc analysis of the BJT circuit:

Find V_C , V_B , V_E , and the mode of operation for both figures 1 & 2 circuits below for $V_{BB} = -5V$, $2.5V$ and $10V$. Also, Find the mode of operation for each V_{BB} . Set the analysis to bias points. Summarized all the values in the tables below.

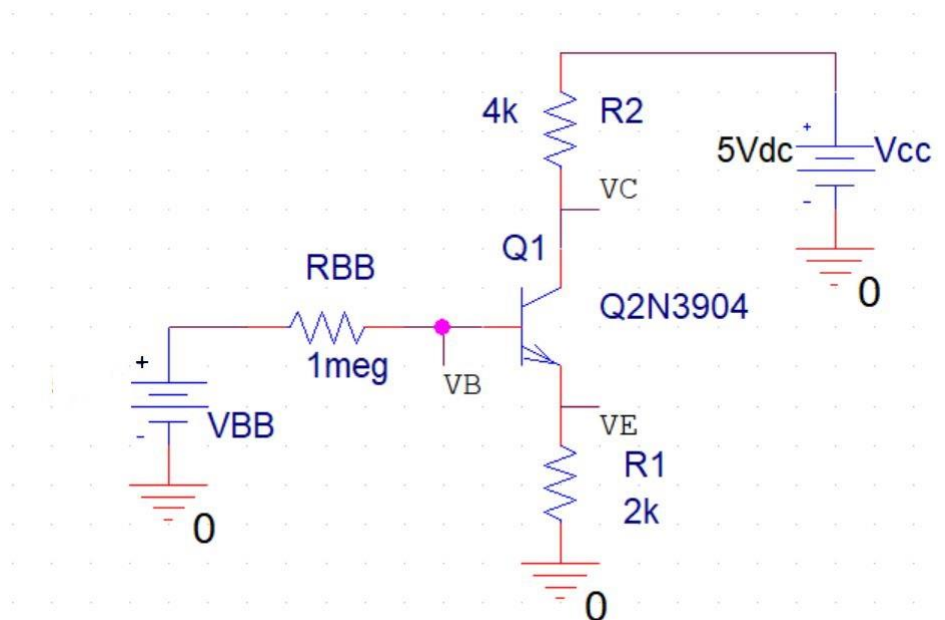


Fig.1

VBB	VC	VB	VE	Mode of operation	Justify your answer
-5V					
2.5V					
10V					

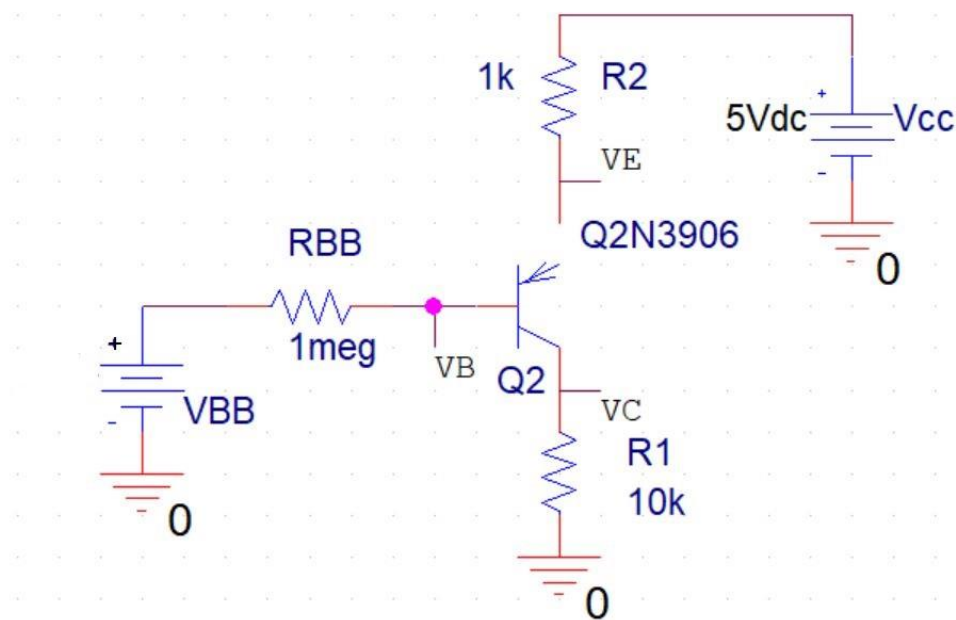


Fig.2

VBB	VC	VB	VE	Mode of operation	Justify your answer
-5V					
2.5V					
10V					

Pre-Spice analysis: (10 points)

- 1- Simulate both figures 1 & 2 circuits using spice OrCAD and show your output simulations.
 - 2- Find V_C , V_B , V_E for both figures 1 & 2 circuits for $V_{BB} = -5V$, $2.5V$ and $10V$. Set the analysis to bias points. Summarized all the values in tables.
-

Discussion:

- 1- For all three BJT transistors used in the lab find (β_{AC} , α_{AC} , r_o) parameters using curve tracer?
-

EXPERIMENT # 6

BJT (Bipolar Junction Transistor) Characteristics



Data sheet

Part (A):

Type	3904(plastic)	3906(plastic)	BC107 (metal)
NPN or PNP			

Part (B):

Calculation using the curves of the curve tracer in the appendix for BJTs characteristics.

Part (C):

VBB	VC	VB	VE	Mode of operation	Justify your answer
-5V					
2.5V					
10V					


Fig.1

VBB	VC	VB	VE	Mode of operation	Justify your answer
-5V					
2.5V					
10V					

Fig.2

Appendix for BJTs characteristics (curve tracer prints out part B):


Transistor INPUT CHARACTERISTICS

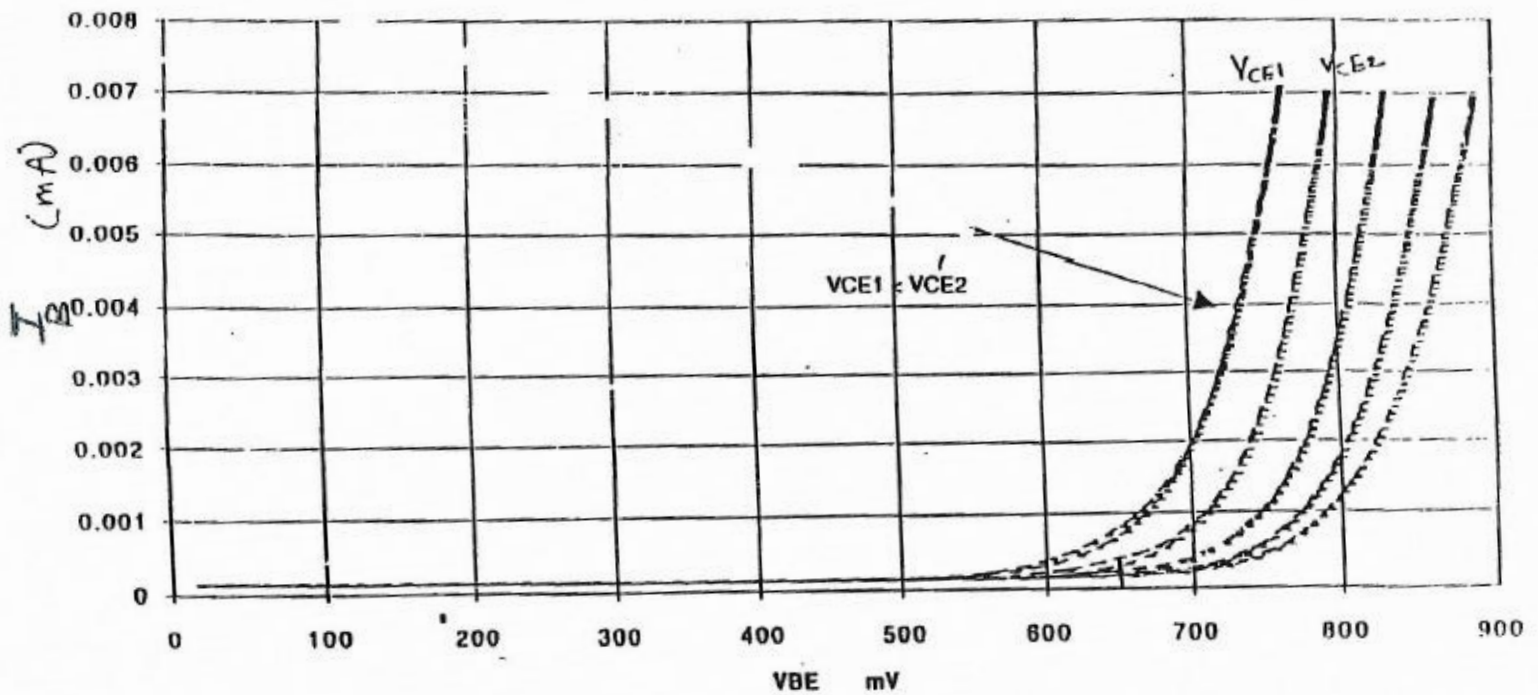

BC 107


TEKTRONIX 571 Curve Tracer

Move cursors **NPN** Pmax = .1 Watt Ib/step = 10 uA Nr of steps = 10
Rload = .25 Ohm

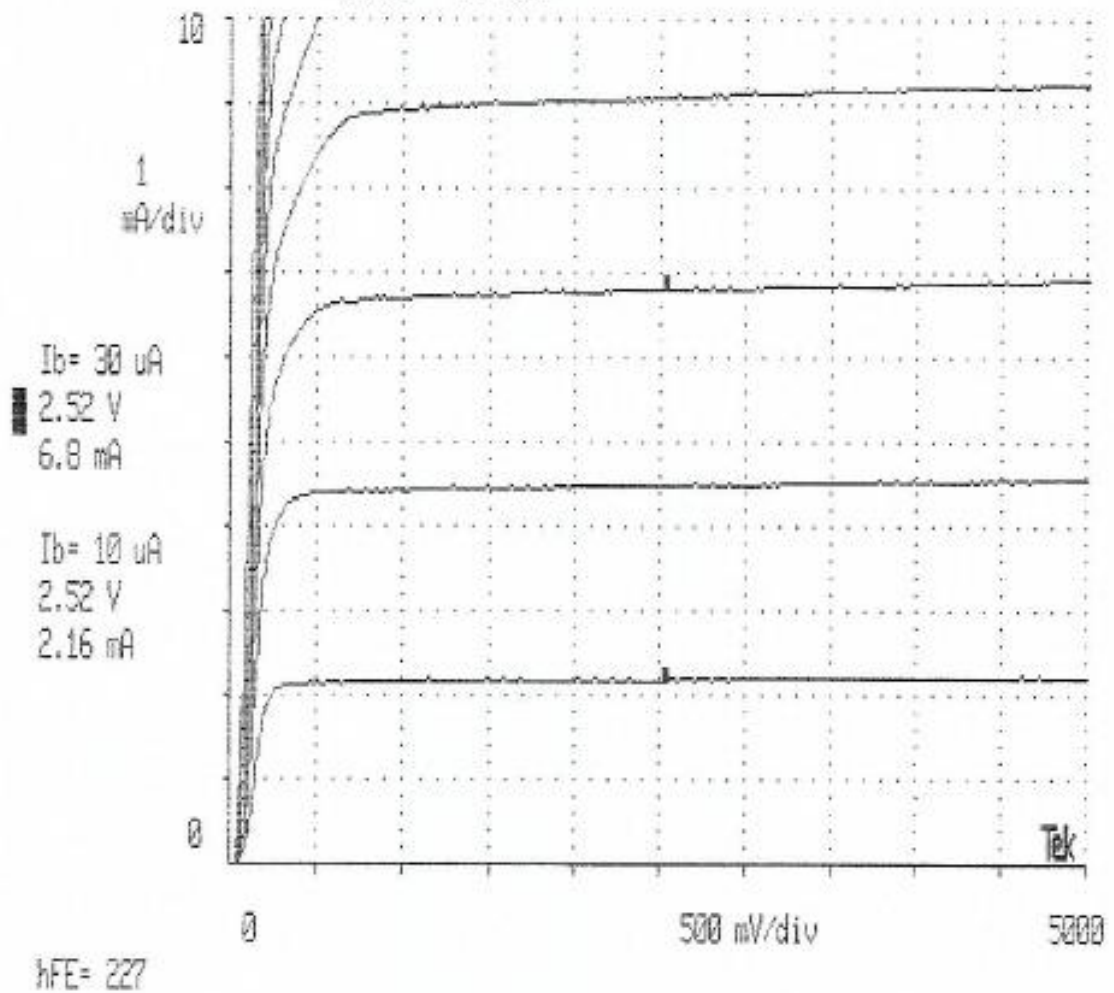

BC 107

TEKTRONIX 571 Curve Tracer

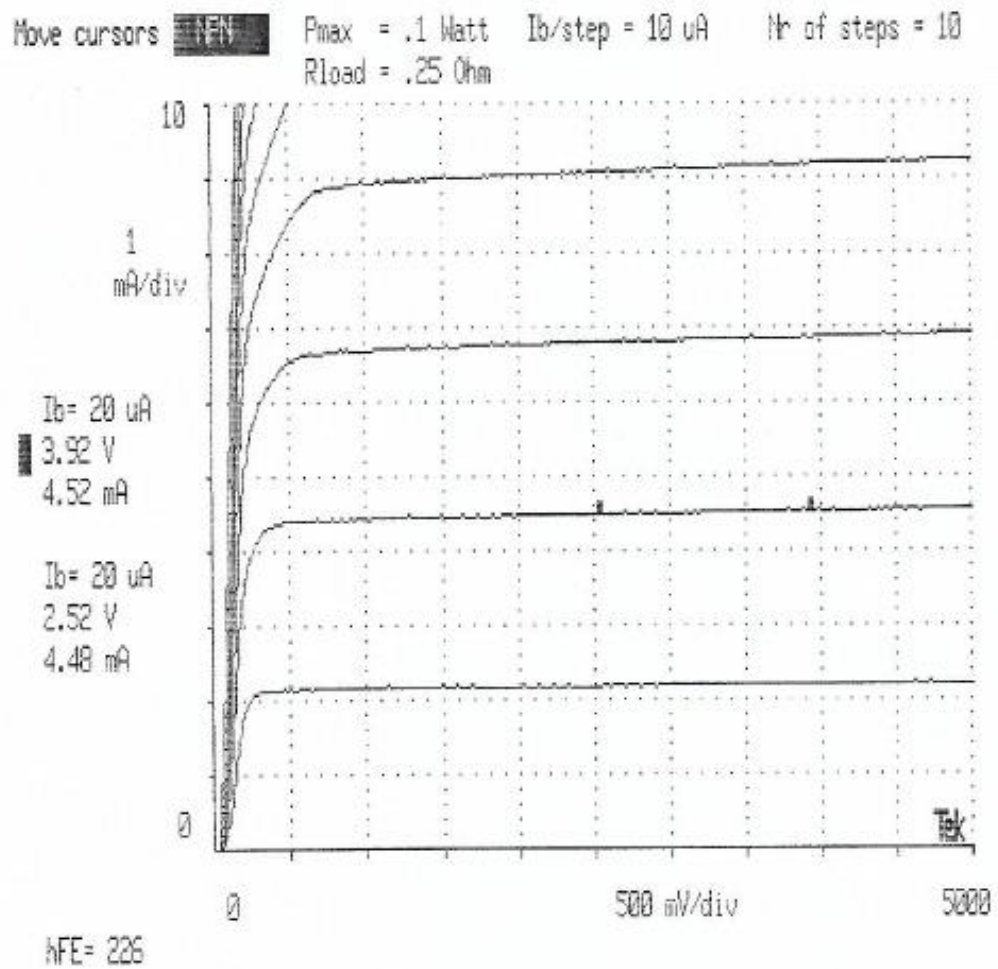


Screen copy (since power up) #2

3904

TEKTRONIX 571 Curve Tracer

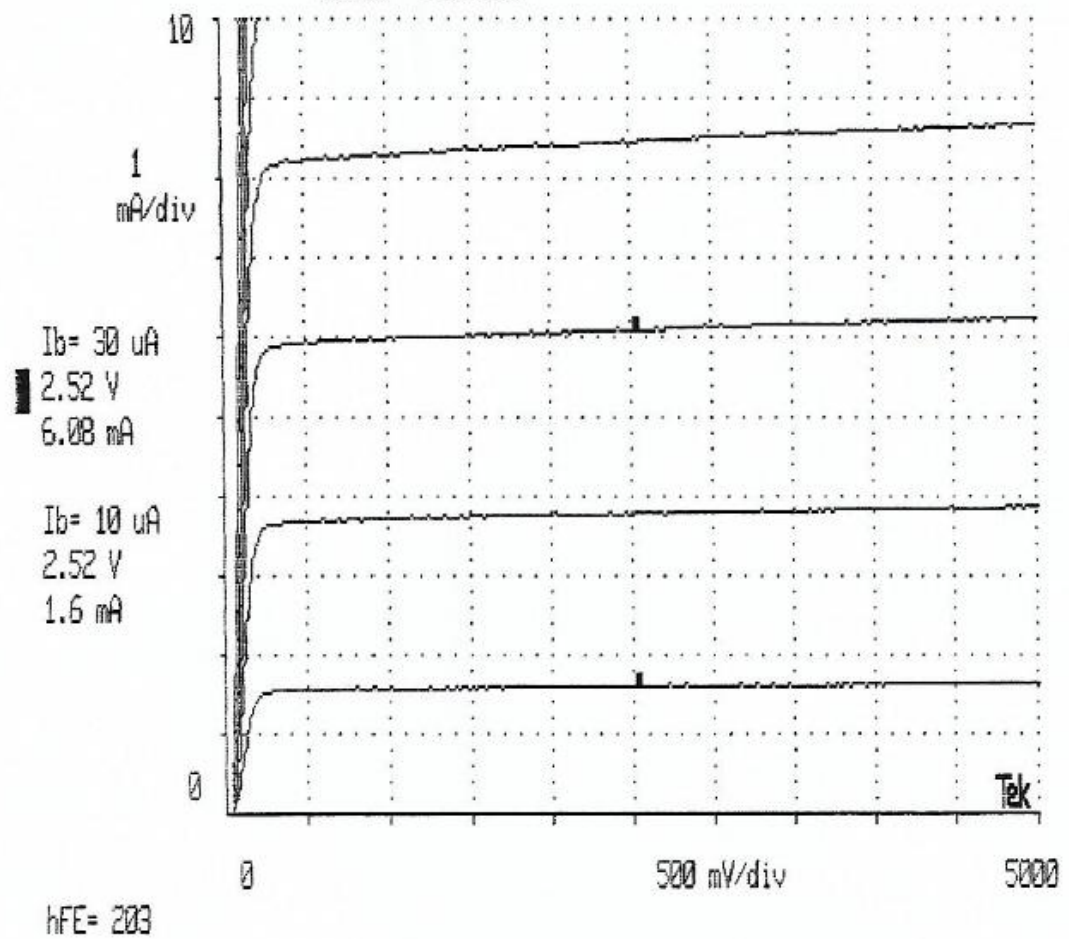
Move cursors **NPN** $P_{max} = .1 \text{ Watt}$ $I_b/\text{step} = 10 \text{ uA}$ $Nr \text{ of steps} = 10$
 $R_{load} = .25 \text{ Ohm}$



3904


TEKTRONIX 571 Curve Tracer

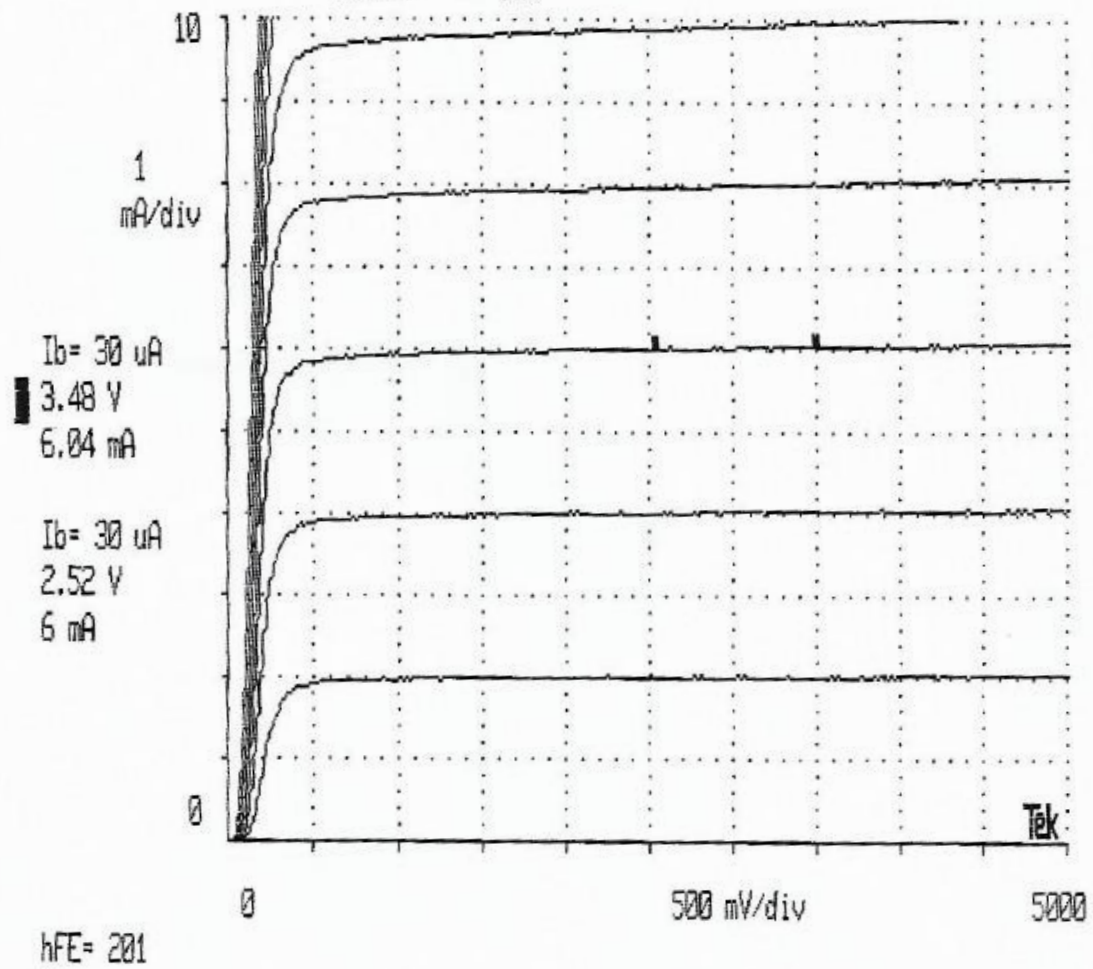Move cursors **NPN** $P_{max} = .1 \text{ Watt}$ $I_b/\text{step} = 10 \text{ uA}$ $Nr \text{ of steps} = 10$
 $R_{load} = .25 \text{ Ohm}$



3906


TEKTRONIX 571 Curve Tracer

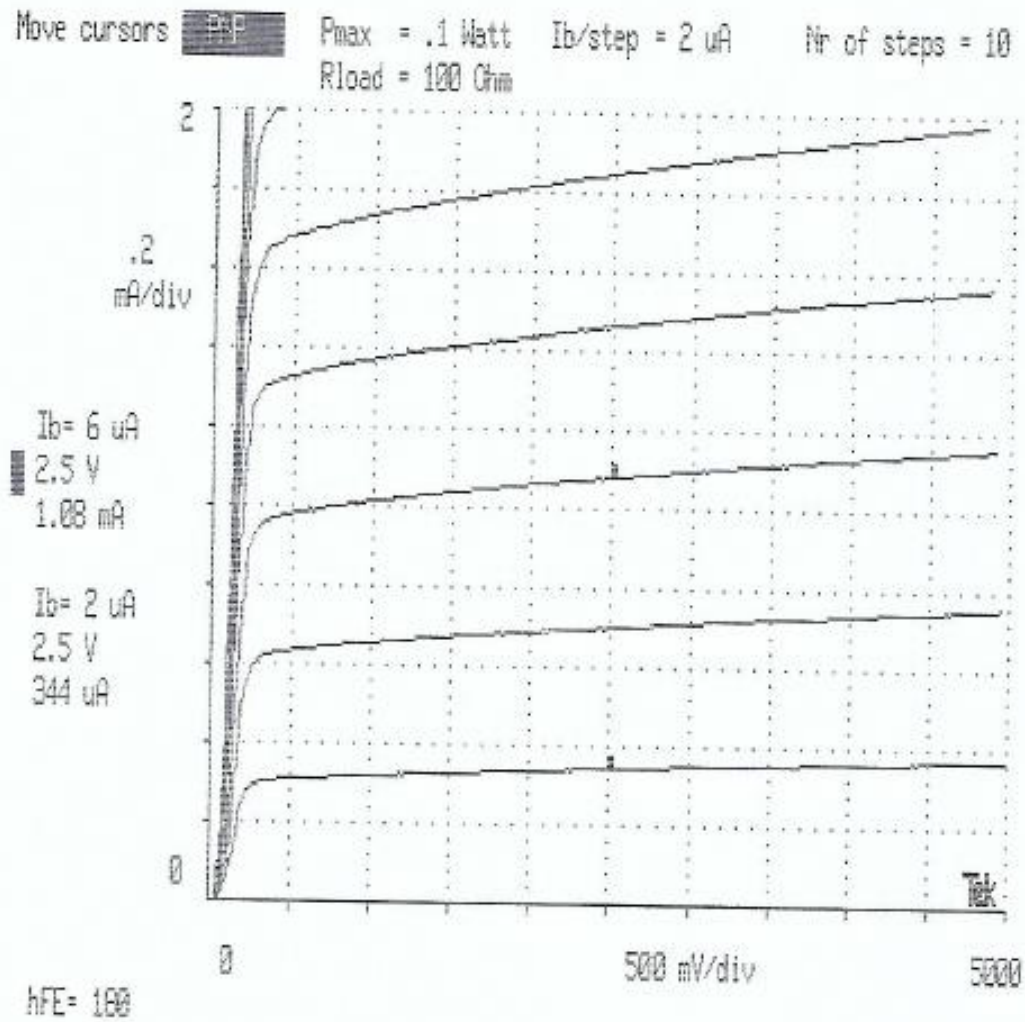


Screen copy (since power up) #1

3906

TEKTRONIX 571 Curve Tracer

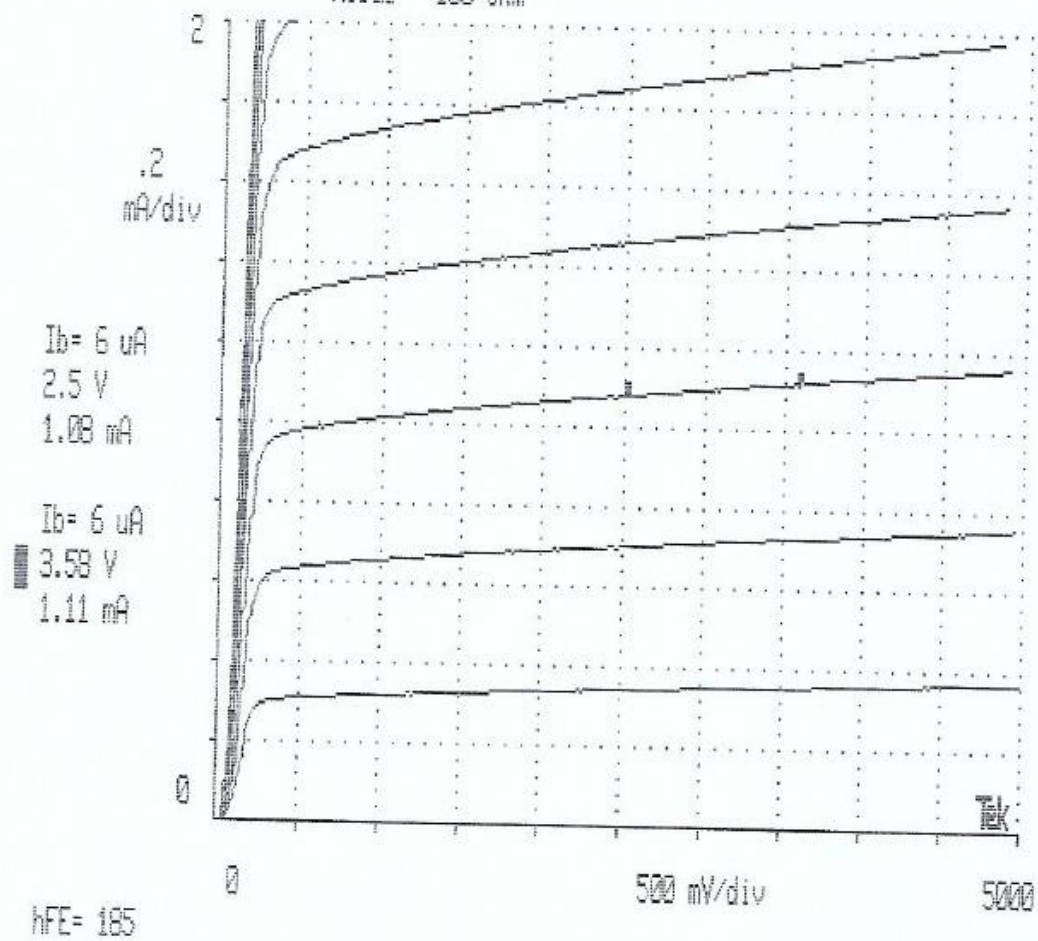Move cursors  Pmax = .1 Watt Ib/step = 2 uA Nr of steps = 10
Rload = 100 Ohm



Screen copy (since power up) #2